

# **CPU Architecture**

**LAB3 assignment**

**Digital System Design with VHDL  
(Multi-cycle CPU design)**

**Hanan Ribo**

**09/06/2024**

## Table of contents

1.	Aim of the Task: .....	3
2.	Assignment definition: .....	3
3.	Controller based system: .....	3
4.	File based simulation of DUT: .....	7
5.	Running Code Example:.....	8
6.	Requirements: .....	9
7.	Grading Policy .....	10

## 1. Aim of the Task:

- System design using concurrent and sequential logic principles using advanced Simulation methods (based on material given in LAB1 and LAB2 tasks).
- Controller design based on methodology of Control and Datapath separation.
- Preparation for LAB4 task – FPGA based design synthesis of a given design.
- Proper analysis and understanding of architecture design.
- Performing and understanding functional validation and verification of an architecture design.

## 2. Assignment definition:

In this task, you are required to design a controller-based processing machine as a Multi-cycle CPU in order to run a given program code. The preparation material for this lab has been learned in the prerequisites course “Central Processing Unit Architecture - theory” until lecture five and includes in addition to the self-learning material given on a subjects of FSM methodology design and advanced functional verification.

## 3. Controller based system:

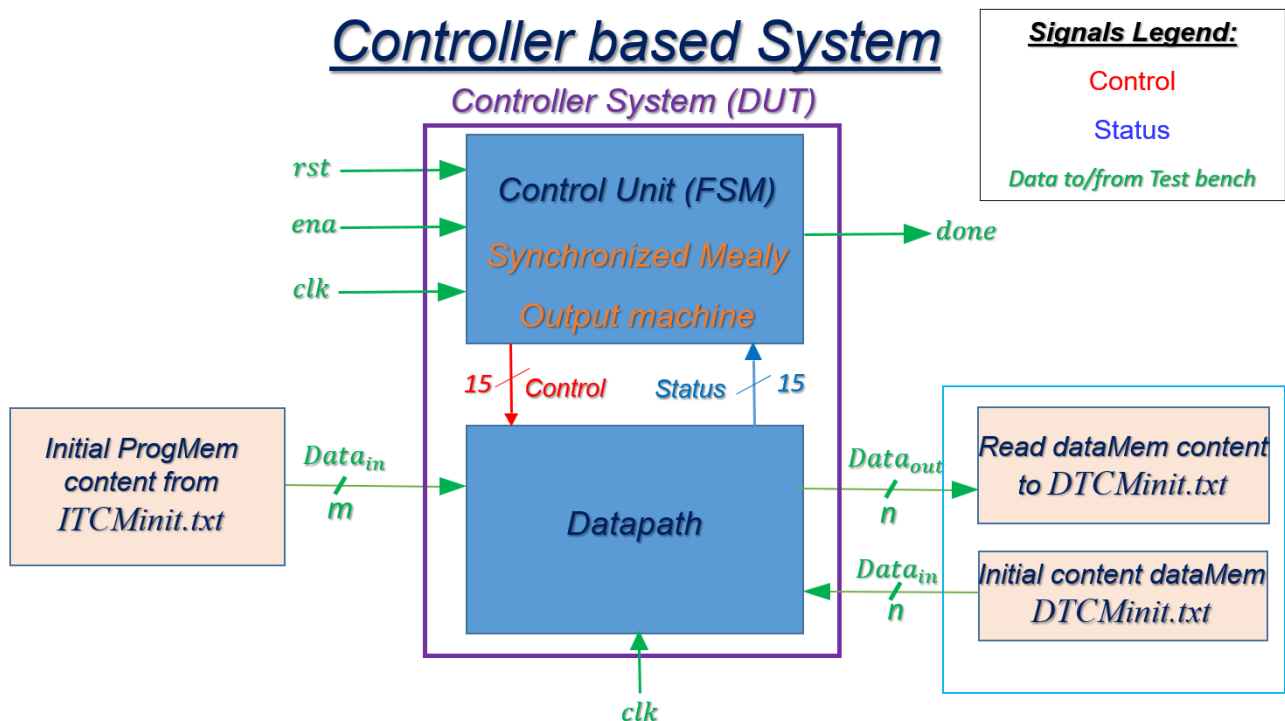


Figure 1: Overall DUT structure

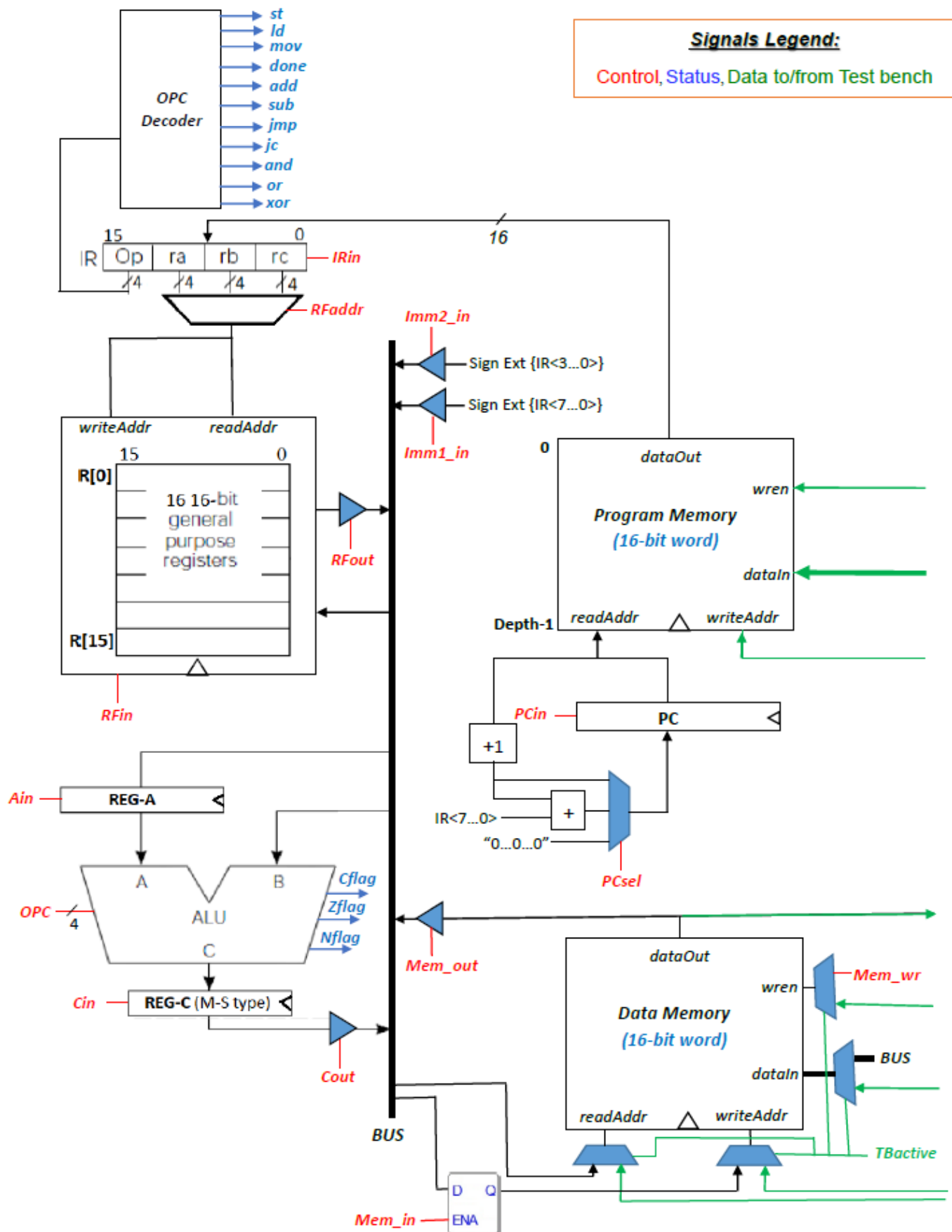


Figure 2: Datapath structure

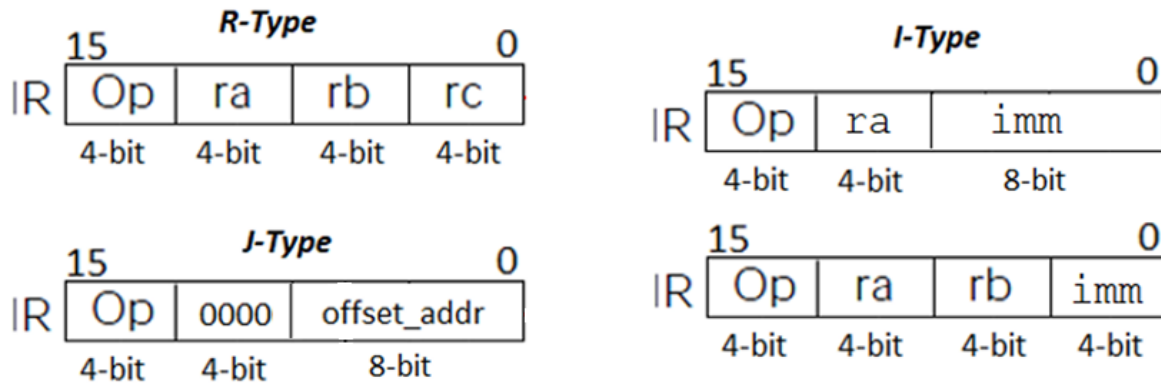


Figure 3: Instruction Formats

Instruction Format	Decimal value	OPC	Instruction	Explanation	N	Z	C
R-Type	0	0000	add ra,rb,rc	$R[ra] \leq R[rb] + R[rc]$	*	*	*
			nop	$R[0] \leq R[0] + R[0]$ ( <i>emulated instruction</i> )	*	*	*
	1	0001	sub ra,rb,rc	$R[ra] \leq R[rb] - R[rc]$	*	*	*
	2	0010	and ra,rb,rc	$R[ra] \leq R[rb] \text{ and } R[rc]$	*	*	-
	3	0011	or ra,rb,rc	$R[ra] \leq R[rb] \text{ or } R[rc]$	*	*	-
	4	0100	xor ra,rb,rc	$R[ra] \leq R[rb] \text{ xor } R[rc]$	*	*	-
	5	0101	<i>unused</i>				
	6	0110	<i>unused</i>				
J-Type	7	0111	jmp offset_addr	$PC \leq PC + 1 + \text{offset\_addr}$	-	-	-
	8	1000	jc /jhs offset_addr	If(Cflag==1) $PC \leq PC + 1 + \text{offset\_addr}$	-	-	-
	9	1001	jnc /jlo offset_addr	If(Cflag==0) $PC \leq PC + 1 + \text{offset\_addr}$	-	-	-
	10	1010	<i>unused</i>				
	11	1011	<i>unused</i>				
I-Type	12	1100	mov ra,imm	$R[ra] \leq \text{imm}$	-	-	-
	13	1101	ld ra,imm(rb)	$R[ra] \leq M[\text{imm} + R[rb]]$	-	-	-
	14	1110	st ra,imm(rb)	$M[\text{imm} + R[rb]] \leq R[ra]$	-	-	-
	15	1111	done	Signals the TB to read the DTCM content	-	-	-

Note: \* The status flag bit is affected , - The status flag bit is not affected

Table 1 : Multi-cycle CPU ISA

# Control Unit

**Signals Legend:** Control, Status, Data to/from Test bench

 


Figure 4: Control unit structure



 


Figure 5: Single Port RAM with an unregistered output (this structure used for Register File and Program Memory with a given VHDL code)

 

**Figure 6: Single Port RAM with a registered output (this structure used for Data Memory with a given VHDL code)**

 - The given files that you must use in your project:




*You are given these source files in complete state*

- ✓ You must use the listed above source files, you are required to fill them up yourself.
- ✓ You can add additional VHDL source code files.
- ✓ Other entities can be designed and modeled behaviorally, structurally, etc.
 
#### **4. File based simulation of DUT:**

- As depicted in figure 1, in order to simulate the system DUT we use file based simulation.
- Two Input and one Output files structure (according the above given figure at clause 3):



## 5. Running Code Example:

```

1  data segment:
2  arr dc16 20,11,2,23,14,35,6,7,48,39,10,11,12,13
3  res ds16 1
4
5  code segment:
6  ld r1,4(r0)
7  ld r2,8(r0)
8  mov r3,31
9  mov r4,1
10 and r1,r1,r3
11 and r2,r2,r3
12 sub r6,r2,r1
13 jc 2
14 add r6,r4,r0
15 jmp 1
16 add r6,r0,r0
17 st r6,14(r0)
18 done
19 nop
20 jmp -2

```

*Assembly  
code*

```

1  int arr[14]={20,11,2,23,14,35,6,7,48,39,10,11,12,13}
2  int res;
3
4  void main() {
5
6      R[1] = arr[4] & 31;
7      R[2] = arr[8] & 31;
8
9      if(R[2] >= R[1])
10         res=0;
11     else
12         res=1;
13
14     loop_forever;
15
16 }

```

*Equivalent  
Pseudo  
code*

1	D104
2	D208
3	C31F
4	C401
5	2113
6	2223
7	1621
8	8002
9	0640
10	7001
11	0600
12	E60E
13	F000
14	0000
15	70FE

1	0014
2	000B
3	0002
4	0017
5	000E
6	0023
7	0006
8	0007
9	0030
10	0027
11	000A
12	000B
13	000C
14	000D
15	0000

1	0014
2	000B
3	0002
4	0017
5	000E
6	0023
7	0006
8	0007
9	0030
10	0027
11	000A
12	000B
13	000C
14	000D
15	0001

*Updated  
values  
after  
program  
run*




## 6. Requirements:

1. The design must be well commented.
2. Elaborated analysis and wave forms:
  - Remove irrelevant signals.
  - Zoom on regions of interest.
  - Draw clouds on the waveform with explanations of what is happening (Figure 4).
  - Change the waveform colors in ModelSim for clear documentation  
(Tools->Edit Preferences->Wave Windows).
3. A ZIP file in the form of **id1\_id2.zip** (where id1 and id2 are the identification number of the submitters, and id1 < id2) *must be upload to Moodle only by student with id1* (any of these rules violation disqualifies the task submission).
4. The **ZIP** file will contain (*only the exact next sub folders*):

Directory	Contains	Comments
DUT	Project VHDL files	<b>Only VHDL files of DUT</b> , excluding test bench <b>Note: your project files must be well compiled without errors as a basic condition before submission</b>
TB	VHDL files that are used for test bench	One <b>tb.vhd</b> for the Datapath One <b>tb.vhd</b> for the Control unit One <b>tb.vhd</b> for the overall DUT
SIM	ModelSim DO files (wave, list)	One <b>tb.vhd</b> for the Datapath One <b>tb.vhd</b> for the Control unit One <b>tb.vhd</b> for the overall DUT (with Datapath and Control unit signals included)
DOC	Project documentation	<ul style="list-style-type: none"> <li>• <b>readme.txt</b> (list of the DUT *.vhd files with their brief functional description)</li> <li>• <b>pre3.pdf</b> (report file that includes brief explanation of the top module with its wave diagrams as shown in figure 4)</li> <li>• <b>designGraph.pdf</b> (elaborated FSM graph of your DUT)</li> </ul>

Table 2: Directory Structure

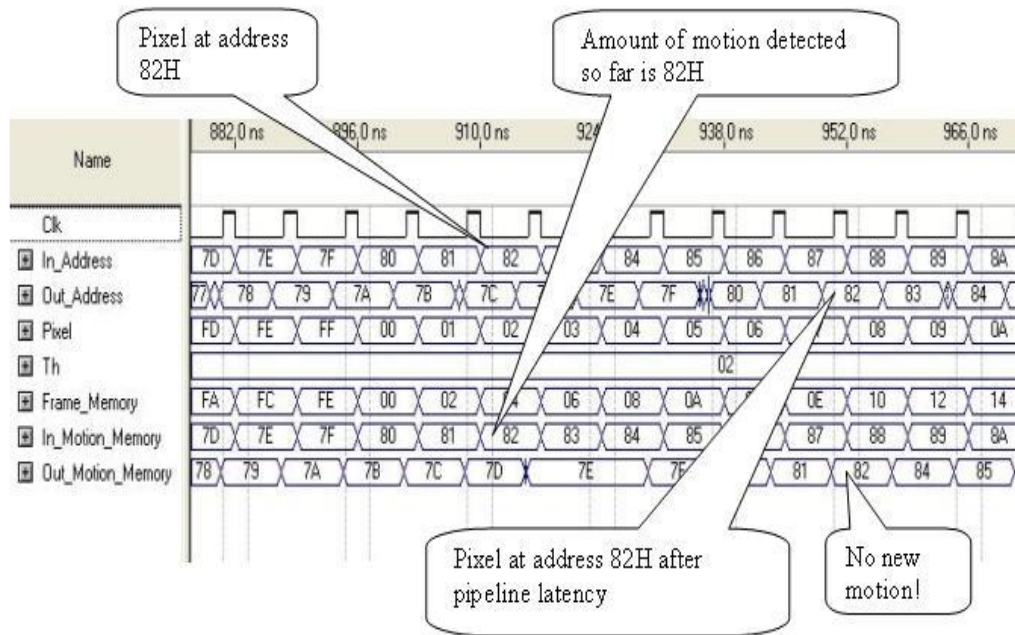

**Figure 4: Clouds over the waveform example**

## 7. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done
90%	Analysis and Test	The correct analysis of the system (under the LAB3 SEAT requirements)

**Table 3: Grading**

Under the above policies you'll be also evaluated using common sense:

- Your files will be compiled and checked, the system must work.
- Your design and architecture must be intelligent, minimal, effective and well organized.